

Architecture et Système

Stefan Schwoon

Cours L3, 2014/15, ENS Cachan

Logical circuits in computer architecture

Several **levels of abstraction**:

physical (transistor) level

logical-gate level


register (word) level

processor level

Static and **dynamic** circuits (time, storage)

Physical level


 
Most computers are built on (various types of) transistors:



Voltage flows from emitter to collector when voltage at base exceeds a certain threshold (“is high”).

Logical gates using transistors

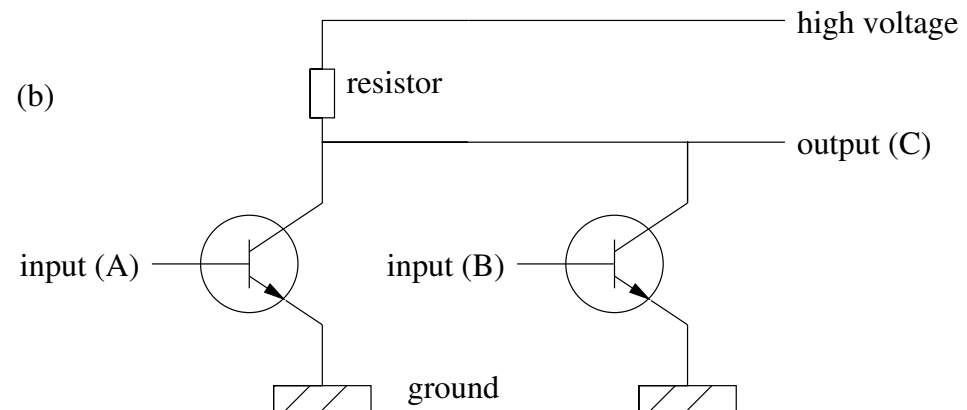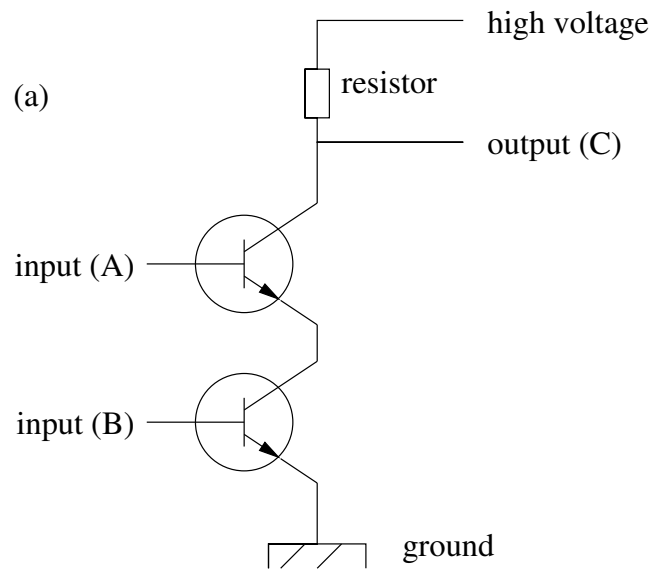NAND (a) and NOR (b) gates built from transistors:



Logical gates

NAND and NOR gates are important for two reasons:

They can easily be realized using transistors.

All other logical functions can be built from either operator, e.g.:

$$\neg A \equiv A \bar{A};$$



$$A \wedge B \equiv (A \bar{B}) \bar{(A \bar{B})};$$

$$A \vee B \equiv (A \bar{A}) \bar{(B \bar{B})}.$$


To abstract from physical details, we use a different type of diagram with [logical gates](#). Here, we are concerned with the treatment of individual bits.

Logical-gate diagrams

  
Diagrams for NAND (left) and NOR (right):



 
Derived logical diagrams, possibly realised by combining several NAND/NOR gates at the physical level:




AND

 

OR

 

XOR

 

NOT

Complexity of logical circuits

Two characteristics are interesting in logical circuits:


the **size**, i.e. how many transistors/gates/wires are present;
this determines the **cost** of a circuit.

the **depth**, i.e. the largest number of transistors/gates on a path between an input and an output; this determines the **speed** of the circuit.


Minimising both size and depth are usually **contradictory** goals!

Complexity and derived diagrams

Consider the XOR gate:

 

 Recall that it is physically realized by, e.g., multiple NAND gates:



The first diagram suggests a size/depth of 1.


The second diagram suggests a size of 4 and a depth of 3.

The number of transistors is 8.

But this may change if only NOR gates are available ...

Complexity and fan-in

 Some functions (AND/OR etc) can be generalised to more than two inputs.



At transistor level, the size and depth can be affected as follows:

if only binary circuits are available, the circuit above can be realized by sequentialising two NAND circuits (4 transistors/depth 2);

if the physical layout allows to sequentialise multiple transistors, then the circuit can be physically realised with 3 transistors and depth 1.

Conventions

In the following, we will be interested by functions of n bits, where n is a variable.

We will wish to know how the size/depth of a circuit realizing a certain function grows as n increases (i.e. their asymptotic complexity).

Typical goal: size $\mathcal{O}(n)$, depth $\mathcal{O}(\log n)$.

Convention: We allow ourselves fixed fan-in (arbitrary, but independent of n) and the previously given logical gates.

At the transistor level, such gates have some constant size and depth (i.e. independent of n).

Thus, the asymptotic complexity at transistor level and at gate level coincide.

Arithmetic functions: Half adder



We first propose a so-called **half adder**:

two input bits, A and B ;

two output bits, C (the *carry*) and S (the *sum*);

desired result: $(C.S)_2 = A + B$ (where $.$ denotes concatenation).

Possible realisation:

 
 


Full adder

A **full adder** produces the addition of three bits, we call the inputs x , y , and c_0 , where c_0 may be the carry of a previous addition.

Desired result: $(c_1.s)_2 = x + y + c_0$

Possible realisation:

  

Other realisations are possible, for instance...?


Adding two integers

Suppose that we have two integers represented as vectors of, e.g., 4 bits.

$$x = (x_3 \cdot x_2 \cdot x_1 \cdot x_0)_2 \text{ and } y = (y_3 \cdot y_2 \cdot y_1 \cdot y_0)_2.$$

We wish to compute the sum $s = x + y$ as $s = (c \cdot s_3 \cdot s_2 \cdot s_1 \cdot s_0)_2$.

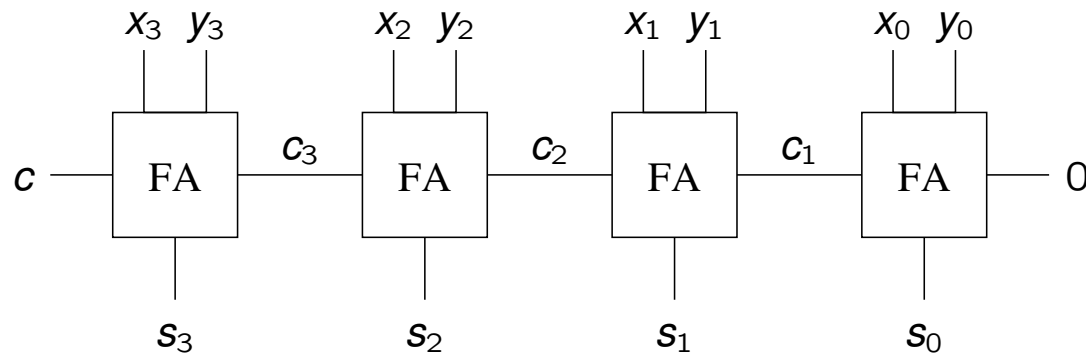Realisation by sequentialising four adders:



Suppose that we generalise the principle of the sequential adder to n bits. Then the size of the circuit is $\mathcal{O}(n)$ and its depth also!

The latter is bad because it would mean that a computer would become (much) slower when its register size is increased.

We shall study a solution with *logarithmic* depth.

Adder based on propagate-generate bits

Let $0 \leq i \leq j < n$. We consider the input bits from position i to j :

the block $i..j$ is said to **generate a carry** if $c_j = 1$ *independently* of the bits at other positions;

the block $i..j$ is said to **propagate a carry** if $c_i = 1$ implies $c_{j+1} = 1$.

Computing these two bits depends only on $(x_i, y_i) \cdots (x_j, y_j)$:


When $i = j$, then $g_{i,j} = 1$ iff $x_i + y_i = 2$ and $p_{i,j} = 1$ iff $x_i + y_i \geq 1$.

Otherwise, let $i \leq k < j$, then:


$$g_{i,j} = g_{k+1,j} \vee (g_{i,k} \wedge p_{k+1,j}) \text{ and } p_{i,j} = p_{i,k} \wedge p_{k+1,j}$$

$$\text{Also, } c_{j+1} = g_{i,j} \vee (c_i \wedge p_{i,j}).$$

 
Symbol for a one-bit full adder extended with p/g bits:



 Symbol for combining p/g bits from two blocks:



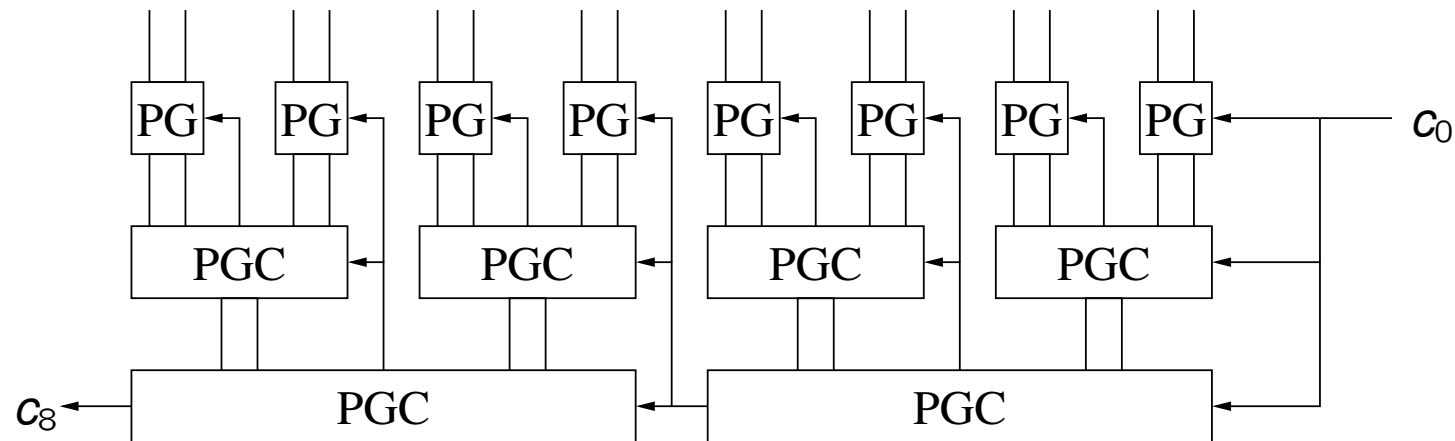Simplified diagram for 8 bits, only the propagation of carries is detailed:



Notice that the p/g bits of an m -th level PGC block are ready after a delay of $\mathcal{O}(m)$. Once the p/g bits *and* the input carry are ready, the output carry can be computed.

The longest path (in terms of PGC blocks) for a carry is approximately $2 \log n$.

Further arithmetic/logical functions

Subtraction, multiplication, division, ...

Comparison, test for zero, ...

Vector-wise AND, OR, XOR, ...

Shifting left or right

Multiplexer: input n bits, select one as output

Decoder: input i , output $y_i = 1$ and $y_j = 0$ for $j \neq i$